
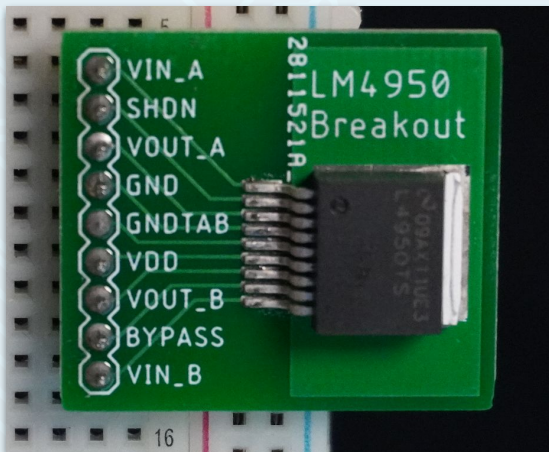
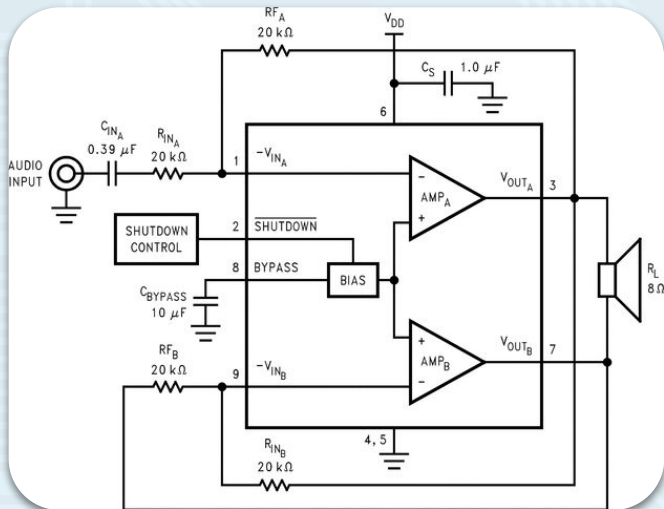




IEEE Projects Amplifier Workshop

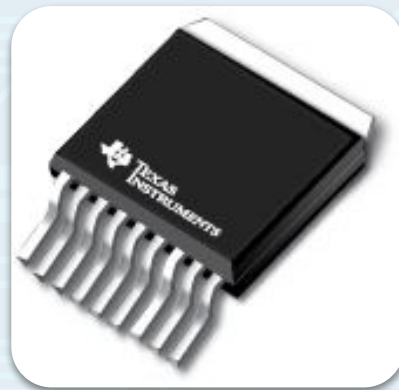

What is an amplifier

Op-amps

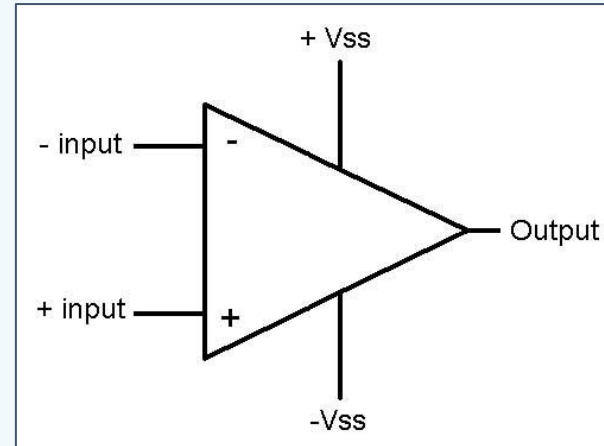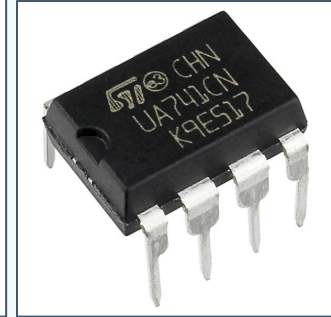- ▶ Invented by Bell Labs in 1940s
 - Only became compact, cheap after transistors
- ▶ Amplifies the difference between two inputs
 - $V_{OUT} = A_{OL}(V_+ - V_-)$
 - V_{OUT} limited by voltage supplied
- ▶ Comparators
 - High-gain op-amp
 - Returns digital signal based on inputs
 - $V_+ > V_- \Rightarrow V_{OUT} = 1$
 - $V_+ < V_- \Rightarrow V_{OUT} = 0$



Top Left: K2-W Op-Amp from Bell Labs

Top Right: The UA741 started the trend of compact, cheap op-amps

Bottom: Simplified pinout of an op-amp

Applications

- ▶ Audio Amplification
- ▶ Oscillators
- ▶ Signal Generators
- ▶ Filters
- ▶ Analog to Digital Converters (ADCs)
- ▶ Digital to Analog Converters (DACs)
- ▶ And More!





Top Right: a stereo audio amplifier using two LM386 op amps
Bottom Left: A Wien-Bridge Oscillator using an op-amp

What IC are we using?

LM4950

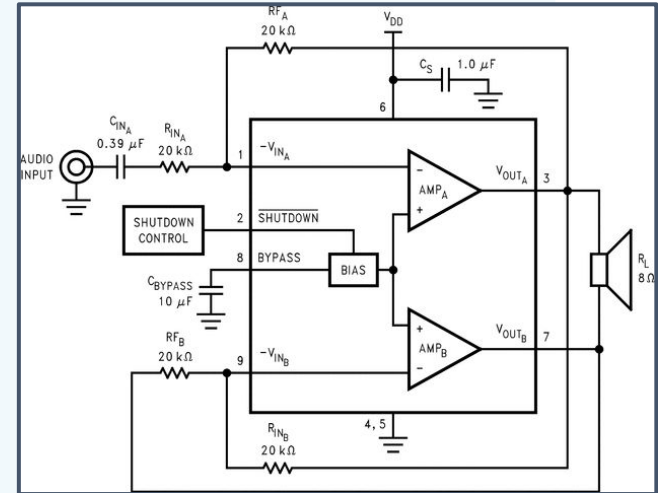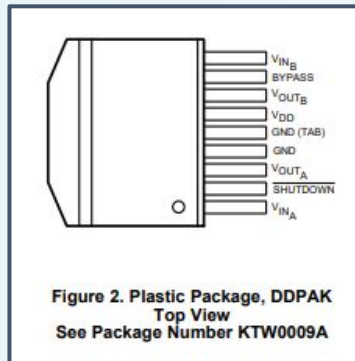- ▶ The LM4950 is designed for sound amplification
 - ‘power amplifier’
- ▶ Composed of two op-amps
- ▶ Two Vin and two Vout for left and right channels
- ▶ Class AB audio amplifier
 - A: lower efficiency but highest sound fidelity
 - B: higher efficiency but worse sound quality



Circuit Overview

- ▶ The LM4950 is permanently configured for an inverting amplifier design!
- ▶ Why would it be configured this way?

